

Power Amplifiers

Class A Amplifier

A **class-A** emitter follower biased with a constant-current source is shown in the following **Figure**. Study the **Figure** carefully. Transistor parameters are: $\beta = 180$, $V_{BE} = 0.7 \text{ V}$, and $V_{CE}(\text{sat}) = 0.2 \text{ V}$. Neglecting base currents, **find**:

- (i) The value of I_Q .
- (ii) The maximum and minimum values of i_{E1} and i_L .
- (iii) The value of R that will produce the maximum possible output signal swing.
- (iv) The conversion efficiency.

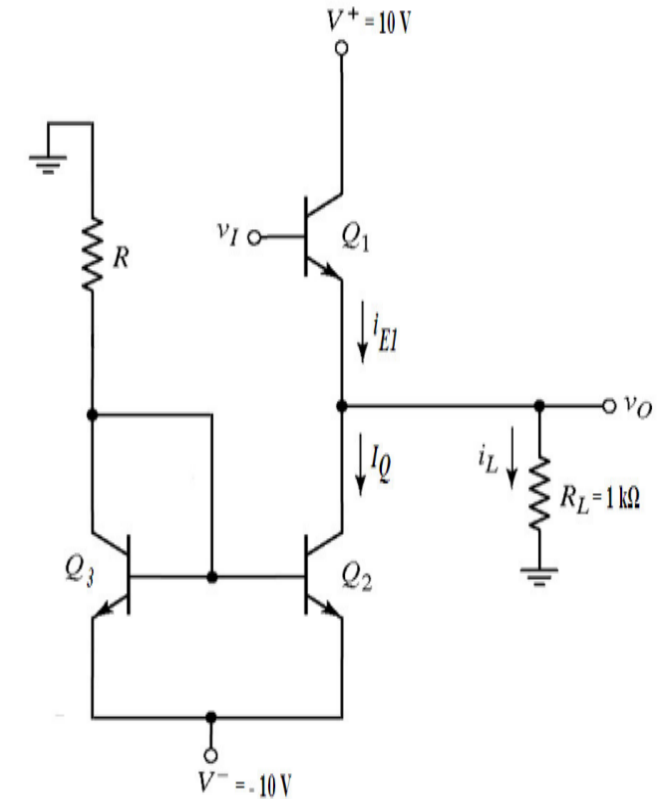


Fig: Output Stage of Class A Amplifier.

(i) $v_O(\text{max}) = V^+ - V_{CE}(\text{sat}) = 10 - 0.2 = 9.8 \text{ V}$
 $I_Q = i_L(\text{max}) = v_O(\text{max}) / R_L = 9.8 / 1\text{k} = 9.8 \text{ mA}$

(ii) $i_{EI}(\text{max}) = 2 I_Q = 19.6 \text{ mA}$
 $i_{EI}(\text{min}) = 0$

$$i_L(\text{max}) = I_Q = 9.8 \text{ mA}$$
$$i_L(\text{min}) = -I_Q = -9.8 \text{ mA}$$

(iii) $R = (0 - V_{BE} - (-10)) / I_Q = 9.3 / 9.8\text{m} = 949 \Omega$

(iv)
$$\bar{P}_L = \frac{1}{2} (i_L(\text{max}))^2 R_L = \frac{1}{2} (9.8\text{m})^2 (1\text{k})$$

$$\Rightarrow \bar{P}_L = 48.02\text{mW}$$

$$\bar{P}_S = I_Q(V^+ - V^-) + I_Q(0 - V^-)$$

$$\Rightarrow \bar{P}_S = 9.8\text{m}(20) + 9.8\text{m}(10) = 294\text{mW}$$

$$\eta = \frac{\bar{P}_L}{\bar{P}_S} = \frac{48.02\text{m}}{294\text{m}} = 16.3\%$$

Class B Amplifier

An idealized class B output stage is to deliver 35 W of average power to a 25Ω load for a symmetrical input sine wave. The maximum output voltage is required to be 80% of the power supply voltage.

- Find the power supply voltage.
- With that power supply voltage, calculate the value of the power conversion efficiency η .

$$P_L^* = 35 \text{ W}, R_L = 25\Omega$$

$$P_L^* = (1/2)(V_P^2/R_L) \rightarrow 35 = (1/2)(V_P^2/25)$$

$$V_P = 41.83 \text{ V} = 0.8 V_{CC}$$

$$V_{CC} = V_P / 0.8 = 52.3 \text{ V}$$



$$P_S^* = (2 V_{CC})(V_P/\pi R_L) = (2 \times 52.3)(41.83/\pi(25))$$

$$P_S^* = 55.7 \text{ W}$$

$$\eta = P_L^* / P_S^* = 35/55.7 = 0.628 \text{ or } 62.8\%$$

Class AB Amplifier

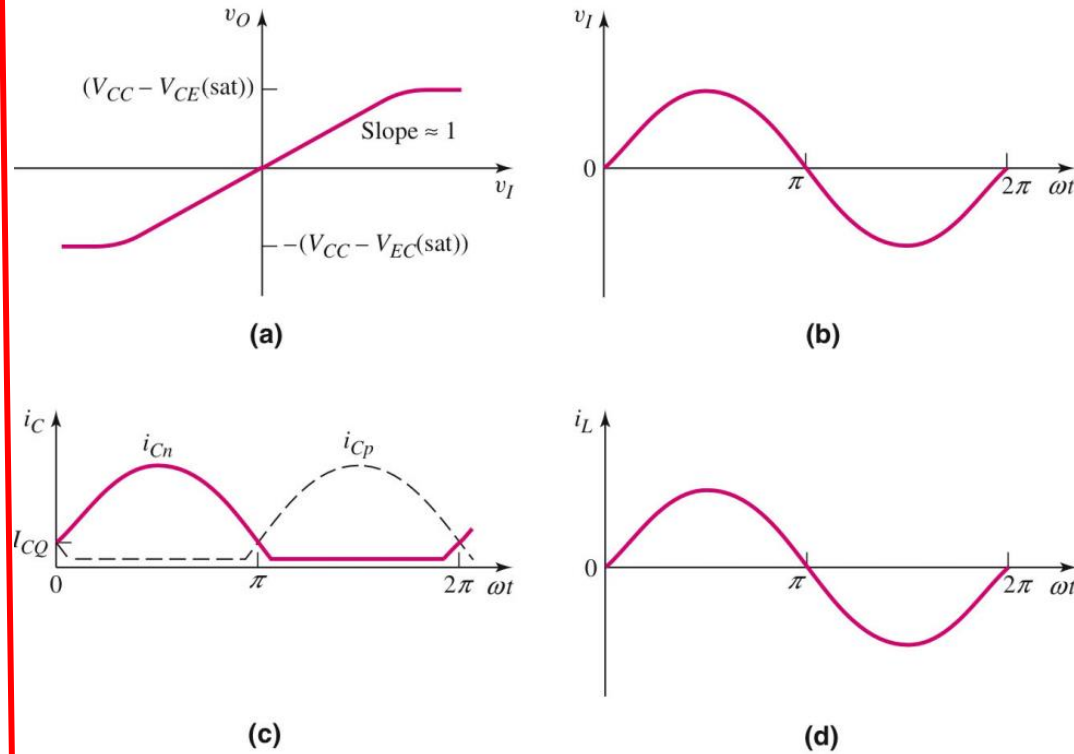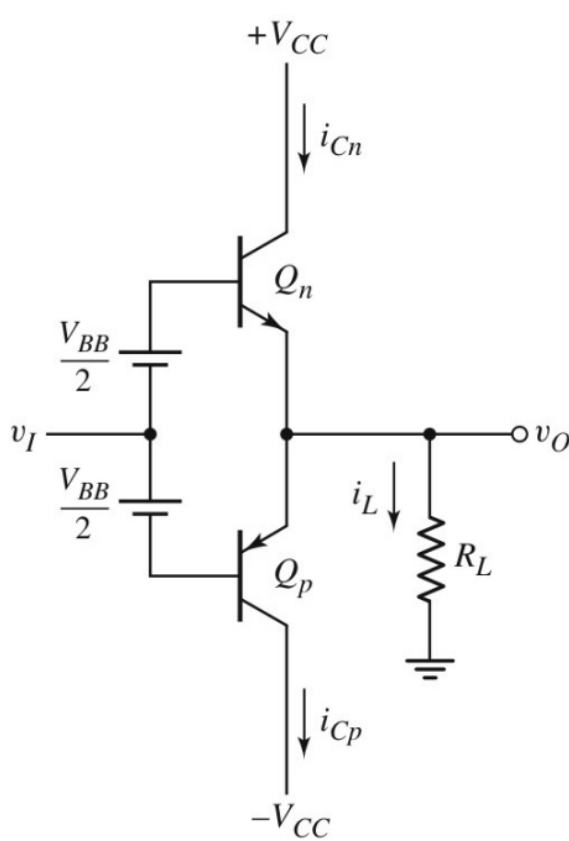❖ Voltage Transfer Characteristics for The Class-AB Output Stage:



- (a) Voltage transfer curve
- (b) Sinusoidal input signal
- (c) Collector currents
- (d) Output current

Fig: Class AB Bipolar Output Stage.

*Thank
you*

