

# *Address Decoding*

- Decoding makes memory function at a unique section or partition of memory map.
- Without an address decoder, only one memory device can be connected to a MP, which make it virtually useless.
- **Why Decode Memory?**
- 2716(EEPROM) has 11 address pin & MP has 20
- means that MP sends out a 20-bit memory address whenever it reads or writes data


# Continued

- Because EPROM has only 11 address pins, there is a mismatch that corrected
- If only 11 address pin are connected to memory, MP see only  $2^{\exp(11)} = 2\text{KB}$  of memory instead of 1MB that it “expects” the memory to contain
- Decoder corrects the mismatch by decoding address pins that do not connect to memory component.

## *Simple NAND Gate Decoder*

- When 2K\*8 RPR0M is used, address connections A0-A10 of MP are connected to address inputs A0-A10 of EPROM
- Remaining 09 address pins (A19-A11) are connected to inputs of a NAND gate decoder
- See fig 10-13, p-348, Brey
- $\overline{CE}=0$ , data will be read from EPROM only if  $\overline{OE}=0$
- OE pin activated by MP,  $\overline{RD}$  signal

Fig 10.13: A simple NAND gate decoder used to select a 2716 EPROM memory component for memory location FF800H-FFFFFH.

 

# Continued


- If 20-bit address, decoded by NAND gate, leftmost 09 bits are 1 & rightmost 11 bits are don't care (X), actual address range of EPROM can be determined
- **Example:** 2 KB EPROM decoded at memory location, FF800H~FFFFFFH

A19	A18	A17	A16	A15	A14	A13	A12	A11	A10	A9	A8	A7	A6	A5	A4	A3	A2	A1	A0
1	1	1	1	1	1	1	1	1	X	X	X	X	X	X	X	X	X	X	X

**Lowest add=1111 1111 1000 0000 0000=FF800H**

**Highest add=1111 1111 1111 1111 1111=FFFFFFH**

# *3-to-8 Line Decoder*

 

**Fig 10.14: Function table for 3-8 line decoder**

[illegible]

# 3-to-8 Line Decoder(74LS138)

- see fig 10-14, p-349,Brey

- for an output(O0-O7) to go low, 03 enable input ( $\overline{G2A}$ ,  $\overline{G2B}$ , & G1) must be active

- to be active,  $\overline{G2A} = \overline{G2B} = 0$ , & G1=1


- once 74LS138 is enabled, address input (C,B,A) select which output pin goes low.

- see fig 10-15, p-350, Brey

- address inputs (C,B,A) connect to MP address pin (A15,A14,A13), determines output pin low & select EPROM



Fig 10-15: Addresses selected in this ckt: F0000H-FFFFFFH.

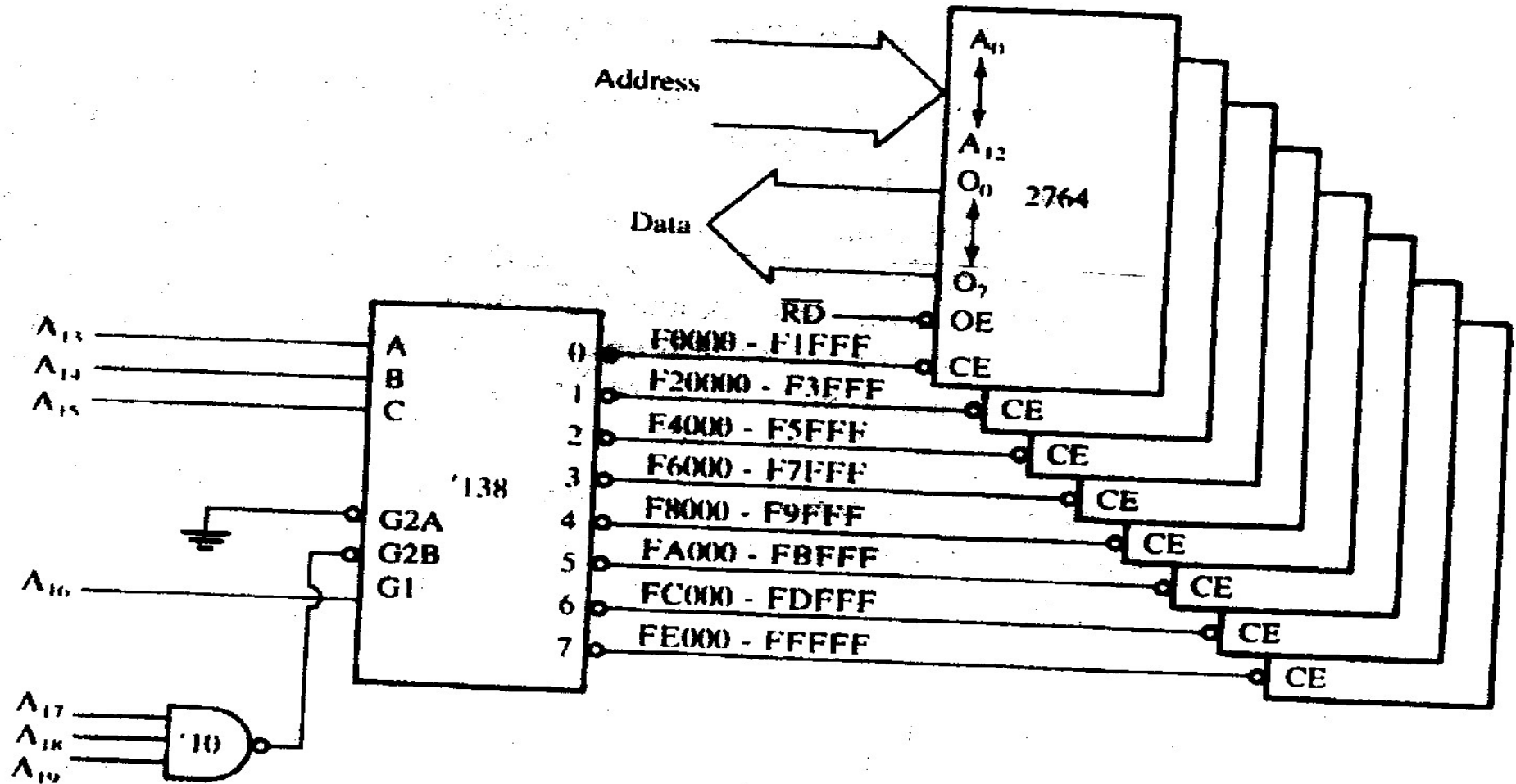

# *Example*

## 01. Addresses range for entire decoder:

A19	A18	A17	A16	A15	A14	A13	A12	A11	A10	A9	A8	A7	A6	A5	A4	A3	A2	A1	A0
1	1	1	1	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X

**Lowest add=1111 0000 0000 0000 0000 =F0000H**

**Highest add=1111 1111 1111 1111 1111 =FFFFFFH**

**Address Range= F0000H~FFFFFFH = 64KB of memory**

# Continued

## 02. For output pin (0):

A19	A18	A17	A16	A15	A14	A13	A12	A11	A10	A9	A8	A7	A6	A5	A4	A3	A2	A1	A0
1	1	1	1	0	0	0	X	X	X	X	X	X	X	X	X	X	X	X	X
				C	B	A													

**Lowest add=1111 0000 0000 0000 0000 = F0000H**

**Highest add = 1111 0001 1111 1111 1111 = F1FFFH**

# Continued

## 03. For output pin (1):

A19	A18	A17	A16	A15	A14	A13	A12	A11	A10	A9	A8	A7	A6	A5	A4	A3	A2	A1	A0
1	1	1	1	0	0	1	X	X	X	X	X	X	X	X	X	X	X	X	X
				C	B	A													

**Lowest add = 1111 0010 0000 0000 0000 = F2000H**

**Highest add = 1111 0011 1111 1111 1111 = F3FFFH**

# ***Problems***

- 01. Design a NAND gate Decoder to select the memory for address range DF800H~DFFFFH.**
- 02. Design a NAND gate Decoder to select the memory for address range 40000H~407FFH.**
- 03. Design a 3-to-8 line Decoder to select the memory for address range 40000H~4FFFFH.**